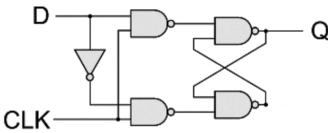


Detailed D Flip-flop


The D Flip-flop is made of a combination of logic gates. One of the combinations is the use of four Nand Gates and a Not Gate. The connections of the gates is as shown in the image below.




Four bit shift register

A simple Shift Register can be made using only D-type flip-Flops, one flip-Flop for each data bit. The output from each flip-Flop is connected to the D input of the flip-Flop at its right. Shift registers hold the data in their memory which is moved or "shifted" to their required positions on each clock pulse. The number of latches in a bit shift register depend on the number of bits to be stored.

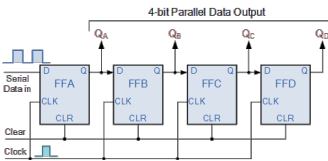The 4 bit shift register looks as shown below



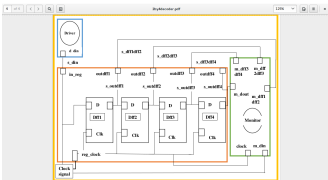Model of Computation used to develop the shift register:



The timing diagram of the 4 bit shift register is as follows

